



Budapest University of Technology and Economics
Department of Electron Devices

Technology of IT Devices

Lecture 10

I/O, clock, data bus

- I/O, realization of input and output
 - Architecture and operation of I/O pads
 - ESD protection
 - Settings of GPIO
- Clock signals
 - Generalization of clock signals
 - Clock signal distribution
- Data bus

I/O circuits

- Responsible for communication with external devices
- Protect chip against overvoltage and electrostatic discharge (ESD protection)
 - If a human touches an IC, the charge/discharge voltage can be a few kV, and the current is a few μA
 - Shock delivered to a chip can fry thin gates of input transistors.
- Drive large off-chip capacitance
 - High current required
 - Usually tri-state buffers with registers
- Power supply and ground pins
 - They provide the required power supply voltage and current
 - In a modern digital circuit there many VDD/GND pins
 - The sum of the switching currents is very high (up to 100A)


Tristate-buffers

■ $En=0$

- PMOS gate 1, NMOS gate 0
- Both transistors are closed, so the output is “floating”
- High impedance

■ $En=1$

 - The input controls the gates.
 - E.g. $In=1$, the output of the NAND gate is 0, the output of the NOR gate is 0.
 - Hence, the PMOS conducts current, and the output is logic 1
- This is called the **PUSH-PULL** stage



ESD protection

■ ESD – Electrostatic Discharge

- It is the sudden flow of electricity between two electrically charged objects
 - Caused by:
 - Contact
 - An electrical short
 - Dielectric breakdown
 - A few kV, but it has low energy.
- ### ■ If an input voltage exceeds the breakdown voltage of the transistor's gate oxide, the transistor can be damaged
- Usually the whole circuit is damaged
 - The breakdown voltage is $\sim 40\text{V}$, but in the case of low voltage circuits it can even be 5V .

ESD protection


- High voltage on the output can cause a short circuit
 - Overheating
 - Total damage of the circuit

- The inputs and outputs are protected against overvoltage and ESD
 - Inside the IC package
 - On the PCB

ESD protection


■ Reminder

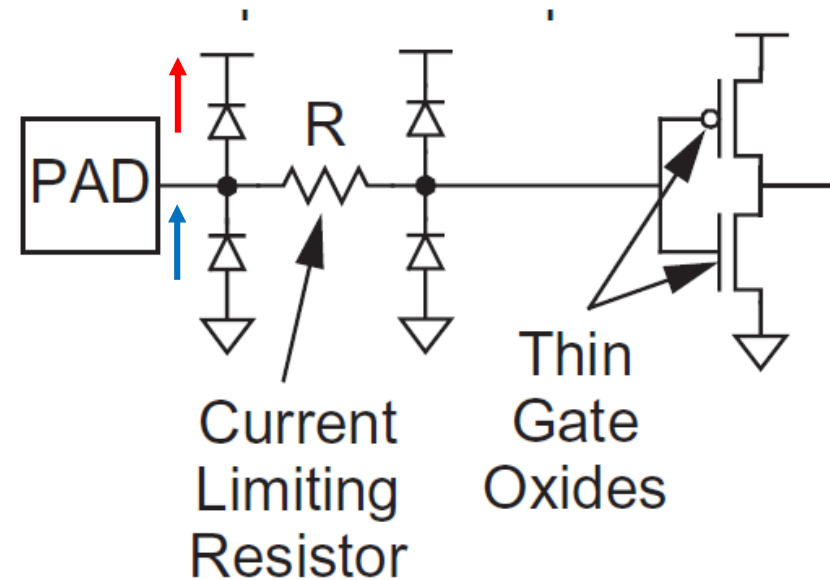- If the anode of a diode is at a higher potential than the cathode, the diode conducts large current
- Otherwise, it doesn't conduct



- The diodes conduct when the input voltage is higher than the power supply voltage, or lower than the gnd voltage
 - The red arrow shows the current if the input voltage is positive
 - The blue arrow shows the current in the case of negative input voltage
 - The diode has $\sim 1\Omega$ series resistance, so the current can be a few 10s of Amps
 - The current is limited by a resistor, and another diode stage is inserted


Human body model

 


- A capacitor of 100 pF is charged to certain voltage, and it is connected to the DUT through a $1,5\text{ k}\Omega$ resistor.
- The rating depends on the maximum survived voltage
 - E.g. ESD 2 – between 2 kV and 4 kV
- ESD protection (external)
 - Antistatic garments (antistatic clothing, shoes etc.)
 - Antistatic floor

Inputs

 - Inputs are generally connected to Schmitt-trigger circuits
 - A Schmitt-trigger is a comparator circuit with hysteresis
 - It has two threshold levels
 - They are typically used in signal conditioning applications to remove noise from signals used in digital circuits
 - The hysteresis is usually $\sim 100\text{-}200\text{mV}$



 (a) A Schmitt-Trigger Squares Up Inputs With Slow Rise and Fall Times



(b) A Schmitt-Trigger Offers Maximum Noise Immunity

Voltage of logic levels


- The voltage of the **core** and the voltage of the I/O pins can be different
 - There are core power supply pins and I/O power supply pins
- In the case of I/O pins there are standard voltage levels
 - 5V (TTL) 3.3V, 2.5V, 1.8V, 1.5V, 1.2V
 - The core voltage is lower...
 - ... and usually it changes dynamically (depending on the computational load)
- The oxide thickness and the threshold voltage of the I/O transistors are different
- The logic voltage conversion has to be solved
 - Level shifter circuits
 - They are the bridges between the two voltage domains

- 11/32

The diagram illustrates the internal architecture of an I/O pin. It is divided into several functional blocks:
Input Driver: Includes an 'Input data register' and a 'TTL Schmitt trigger'. It receives signals from 'To on-chip peripheral' and 'Alternate function input'.
Output Driver: Includes an 'Output data register' and an 'Output control' block. It is controlled by 'Read', 'Write', and 'Read/write' signals. The 'Output control' block drives a 'P-MOS' and 'N-MOS' transistor pair.
Protection and Configuration: The I/O pin is protected by two diodes connected to $V_{DD_FT}^{(1)}$ and V_{SS} . It also features pull-up and pull-down resistors. The output mode is configured as 'Push-pull, open-drain or disabled'.
External Connections: The pin is connected to 'Analog' signals and 'Alternate function output' lines.
Power and Ground: The circuit is powered by V_{DD} and V_{SS} .


The input settings

- VDD_FT, 5V tolerant input,
 - It means that the pins can be driven up to a 5V logic level without damage or sinking current through protection diodes
 - The VDD voltage of the diode is connected to a higher potential (V_{DD_FT})
- The input is connected to a Schmitt trigger circuit which has a hysteresis of 5% or 100mV minimum.
- There are configurable pull-up and pull down resistors with values of $\sim 40k\Omega$
 - We can fix the logic level (e.g in the case of interrupt request pin)
 - The unused pin has to be grounded

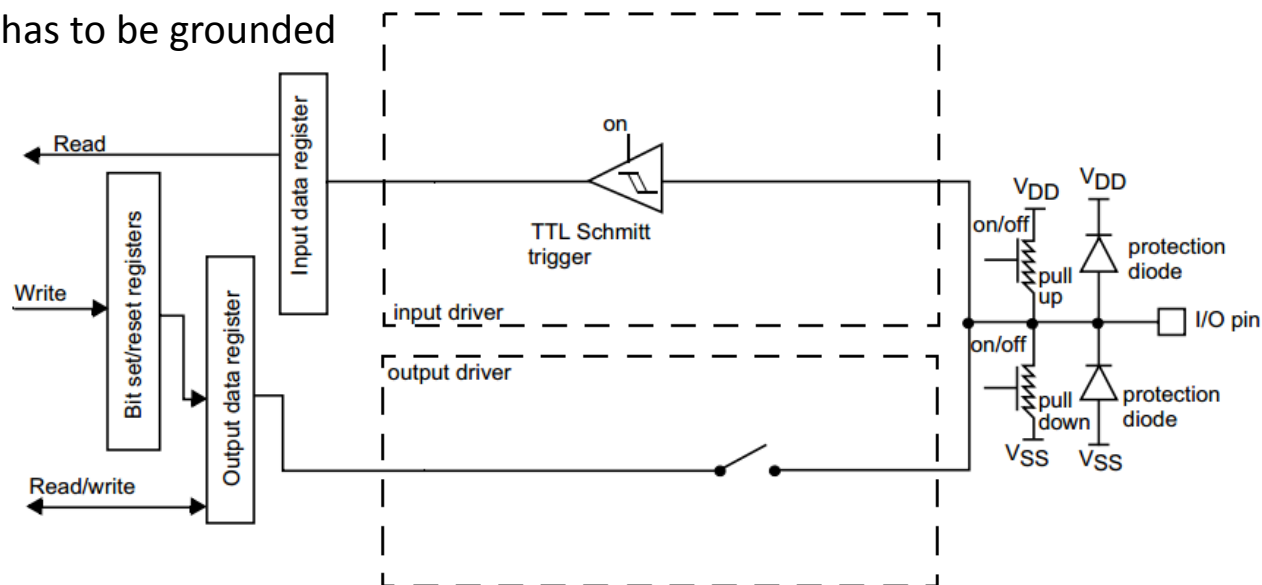

The output settings

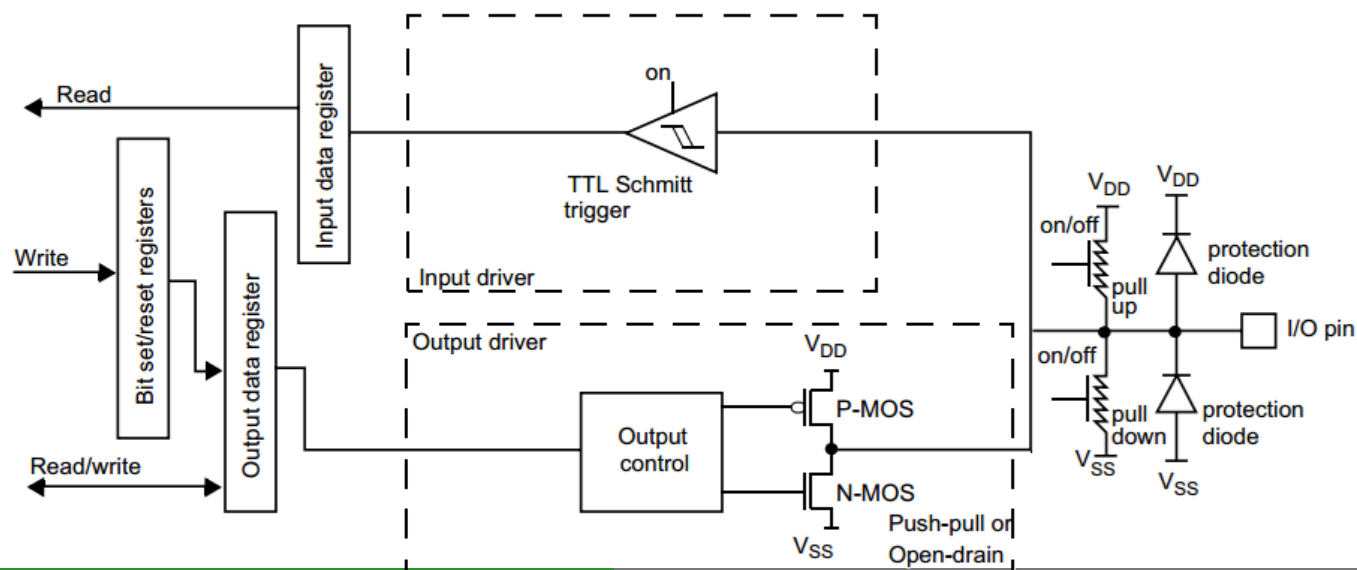
- The output can be a push-pull stage
 - Either the NMOS or the PMOS conducts
 - It connects the output to the power supply or to the ground
- Open drain (or open collector – in TTL cases)
 - Only the NMOS is driven
 - It can only sink current (force 0)
 - More than one output pin can be connected to one input pin (\overline{IRQ})



Open-drain output

■ A single NMOS transistor is controlled

- If the transistor is open-circuit, there is no current, the output is connected to VDD through the resistor
- If the transistor conducts current, this circuit becomes a voltage divider
- If the resistance of R is high enough, and the channel resistance of the transistor is low, the output voltage is around 0V (but not exactly 0)
- If the output is low, current flows between VDD and the ground
 - This causes static power consumption!

 

Further I/O settings


- Maximum output current (fanout)
 - Power saving: use the minimum sufficient current setting.
 - E.g. 10mA, 5mA or simply low/high strength
- Slope of the output (speed)
 - Slew rate.
 - $SR = \left. \frac{dV}{dt} \right|_{MAX}$
 - V/μs is the usual dimension
 - The faster the output the higher the noise
 - To decrease the noise the lowest acceptable SR has to be set

Clock signals

- Today's digital circuits have synchronous operation
 - The asynchronous circuits are more efficient and faster, but there are a lot of design challenges (like race conditions). And there are no logic synthesizers...
- Increasing the size of a chip results in longer clock signal paths on the surface of the integrated circuit
- The clock signal:
 - Switching probability = 1 (it always works)
 - It operates at the highest frequency
 - It is connected to almost all the cells in the case of ASIC and FPGA too
 - It causes ~40% of the power consumption
 - Power saving: clock gating, dynamic frequency scaling

■ Clock signal distribution

- Clock distribution networks synchronize the flow of data signals among synchronous data paths
- It distributes the clock signal(s) from a common point to all the elements that need it
- Uncertainty in the arrival times of the clock signals can limit the maximum performance of the entire system
- The most effective way to get the clock signal to every part of a chip that needs it, with the lowest skew, is a metal grid.
- It can be a symmetrical, tree-topology network
- Clock skew: a phenomenon in synchronous circuits in which the same clock source signal arrives at different components at different times.
- The clock skew has to be lower than 5%
 - @3GHz it is 16ps!

 

Clock signal generation



■ Oscillators

- It is an electronic circuit that produces a periodic, oscillating electronic signal
- (e.g. a ring-oscillator (Lecture 3))

■ RC oscillator

- The oscillating frequency depend on the resistor and capacitor ($f=1/(2*\pi*R*C)$)
- In the case of integrated circuits it is not so precise (due to the variation of the resistance)
 - It requires calibration (after production or during operation)
- The precision: 0.01%-1% (again it is not enough, and the frequency is temperature-dependent)
- Fast startup
- In the case of an external oscillator the chip starts using the internal oscillator, and after a while the chip switches to external one

A simple RC oscillator

  

■ A Schmitt trigger based circuit

- Assume that the voltage of $C1$ is 0V
- The output of the inverter is VDD, the capacitor is charging through the resistor $R1$
- If the voltage of $C1$ reaches the threshold level, the inverter switches, and $C1$ discharges through $R1$
- Until the lower threshold level, when the output of the inverter becomes logic one again

Resonators

- Crystal (quartz) or ceramic resonator
- It has piezoelectric effect
 - The electric charge that accumulates in certain solid materials in response to applied mechanical stress.
 - The quartz crystal has a precisely defined natural frequency (caused by its shape and size) at which it prefers to oscillate.
- The natural frequency can be set by the shape and size of the quartz crystal
 - Precision: ± 10 -100 ppm (parts per million)
 - E.g. a quartz of 4MHz with the precision of 10ppm: the output frequency is between 3 999 960 and 4 000 040Hz
 - The temperature dependency is low: 1-10ppm /°C
 - (sometimes this precision is not enough, so there are temperature controlled oscillators – OCXO)


Commonly used crystal frequencies

■ Most important frequencies:

- 32,768kHz – for all RTC (real time clock)
- 8MHz, 10MHz, 20MHz, 25MHz – for general purposes
- 11.0592MHz – UART
- 12MHz – USB, CAN
- 27MHz – PAL, NTSC television techniques...
- Etc.




Phase-locked loops (PLL)

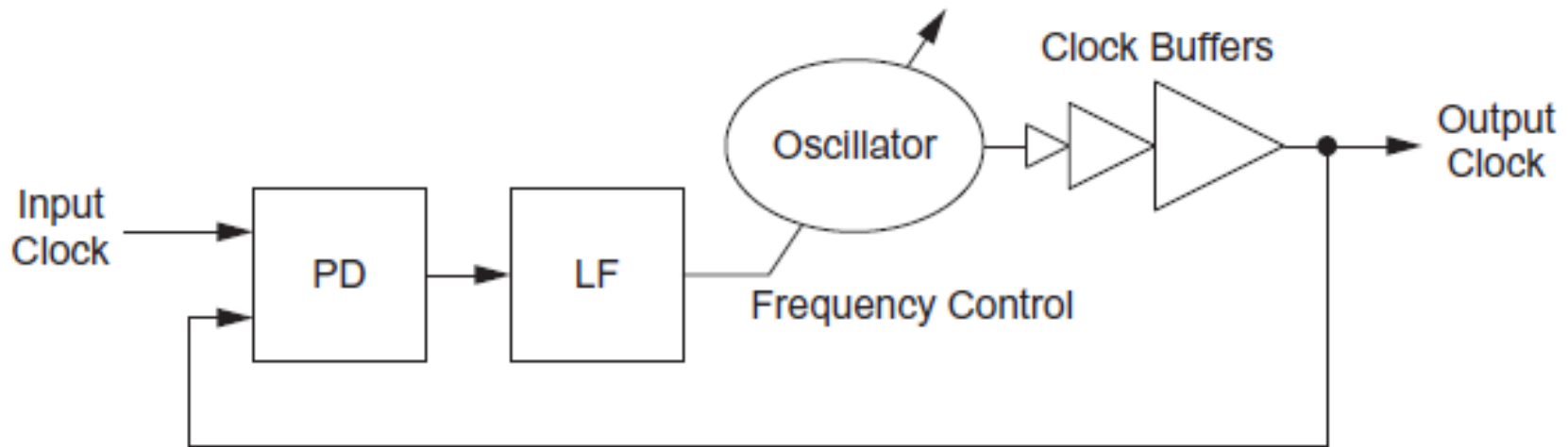

- It generates an output signal whose phase is related to the phase of an input signal
- It can generate a frequency that is a multiple of the input frequency
- Phase-locked loops are widely employed in radio, telecommunications, computers and other electronic applications.

PLL – frequency synthesis

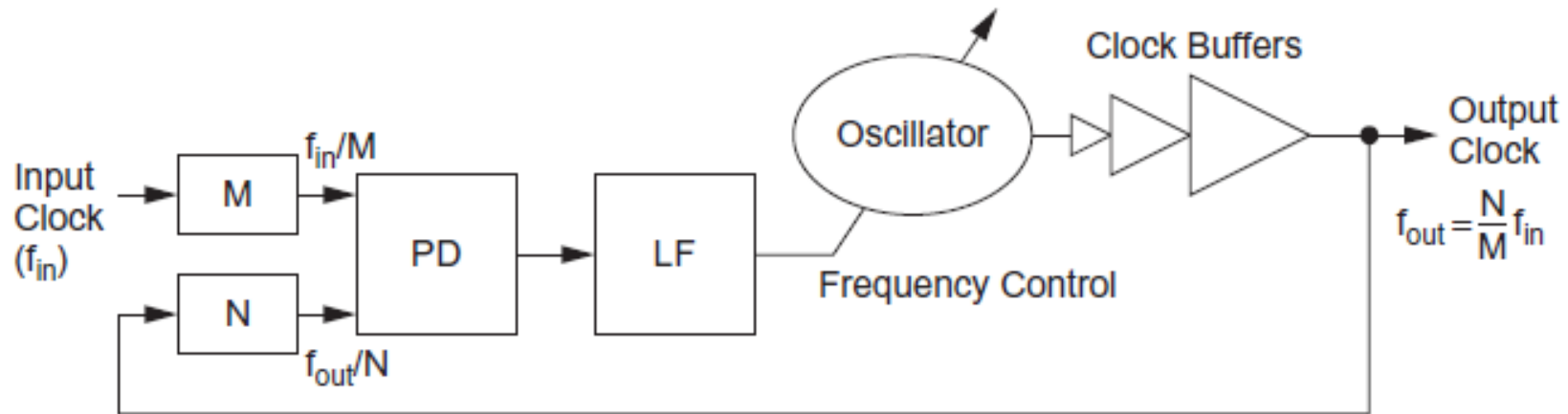


- Basic elements:
 - Frequency dividers (M and N)
 - Phase detector (PD): generates a voltage signal which represents the difference in phase between two input signals
 - Low pass filter (LF)
 - Variable-frequency oscillator (mostly voltage controlled oscillator)
- It generates a frequency that is a multiple of the input frequency

Digital communications


- Communication on a single chip is not so complicated and challenging
 - The real bottleneck can be found out of ICs
- The most problematic fields
 - Communication between ICs
 - Communication between PCBs
 - Communication between devices
- High bandwidth is required
 - But the power consumption has to be low
 - With low electromagnetic interference (EMI).
 - And with simple cabling or **wireless**

Example: displays

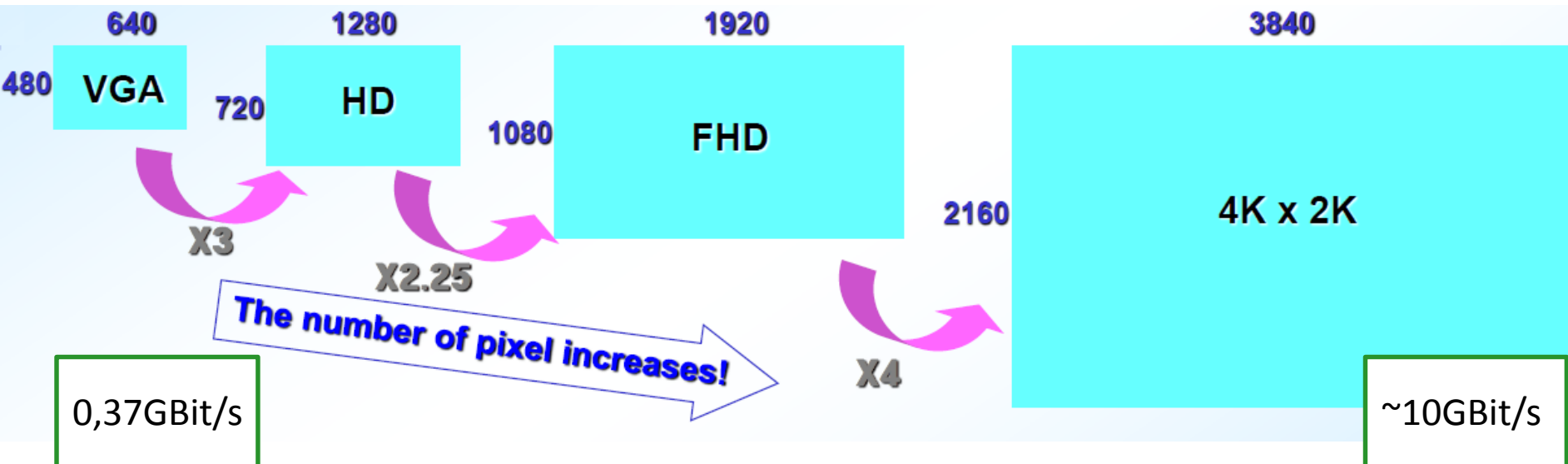


- The bandwidth requirement is 27×
 - From the VGA monitor to a 4K display

Parallel data bus.

 

- Direct connection (there is no data link layer, packet etc.)
- Easy to implement
- It requires a clock signal
- It occupies a huge chip area and lots of wires are required


Logic signal transfer

 

- At low frequencies it is easy to transmit the usual logic levels (0 and VDD)
 - This is called **single ended** data transfer (as you can see in the picture above)
- It can be problematic when the periodic time is close to the propagation delay
 - The speed of the signal is exactly equal to the speed of light
 - $v = c / \sqrt{\epsilon_r \mu_r}$

- Example: 10cm long wire on a PCB
 - $v = 3 \cdot \frac{10^8}{\sqrt{4,35}} = \frac{14,4cm}{ns}$
 - It takes 700ps to go 10cm.
 - If we suppose that the rising edge and the falling edge of the signal is the quarter of the periodic time, we got a signal with periodic time of 2.8ns.
 - It means the maximum frequency is 350MHz.
- In the case of parallel buses the length of the wires has to be perfectly equal!
- Anyway, they arrive at different time at the receiver
- It is difficult to maintain the signal integrity due to the inductance and capacitance of the wires
 - Furthermore, cross coupling occurs.
- This is the main drawback of the parallel communication

Serial data transfer

 

- Simple electronic connection (less wiring)
- The clock signal is embedded into the data
- Longer cables are possible because there is no data or clock skew.
- But the communication protocol is more complicated

- Based on its advantages, serial communication became the dominant data transfer solution
 - If the bandwidth is not enough, more serial channels can be used
 - Differential signal transfer (noise immunity)
 - The clock signal originates from the transferred data, or clock recovery packets are used
- For example: PCI Express, SATA, USB, HDMI etc.
- Practically, you can find serial data buses everywhere (except the memory bus)
- Physical layers:
 - LVDS (Low voltage differential signaling)
 - CML (Current mode logic)



LVDS and CML signal levels

