



Budapest University of Technology and Economics
Department of Electron Devices

Technology of IT Devices

Lecture 7

Memory (Part 1)

RAM memory

Memory

- Overview
- MOS transistor – recap and its operation in more detail
- Random Access Memory (RAM)
 - Static RAM
 - Dynamic RAM
- Content Addressable Memory (CAM cells)
- Novel memory architectures
- Examples

Semiconductor memory – basic term

■ $M \times N$ memory


- M times N bit wide memory words. M is a power of two, N is a multiple of 8.
- E.g.: $64k \times 16$ means a capacity of 1Mbit

■ (Traditional) Types of Memory


- ROM vs. RAM, read-only vs. Read/write memory
- The names are confusing
 - EEPROMs are read/write memory, the information in NVRAM is preserved after the power supply voltage is switched off.

■ Better classification:

 
- Read-only vs. Read/write
- Data storing time interval



Semiconductor Memory Classification

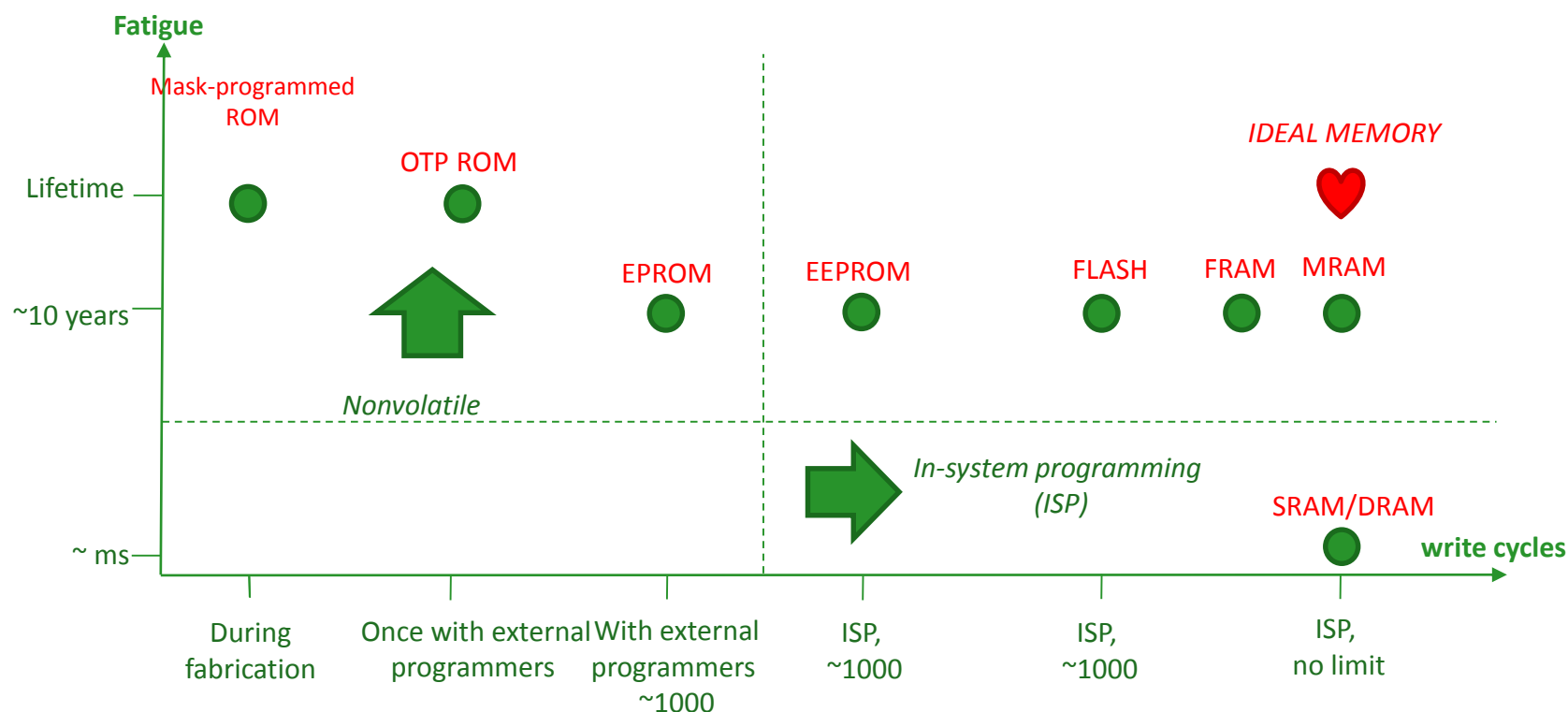


Typical Memory Architecture

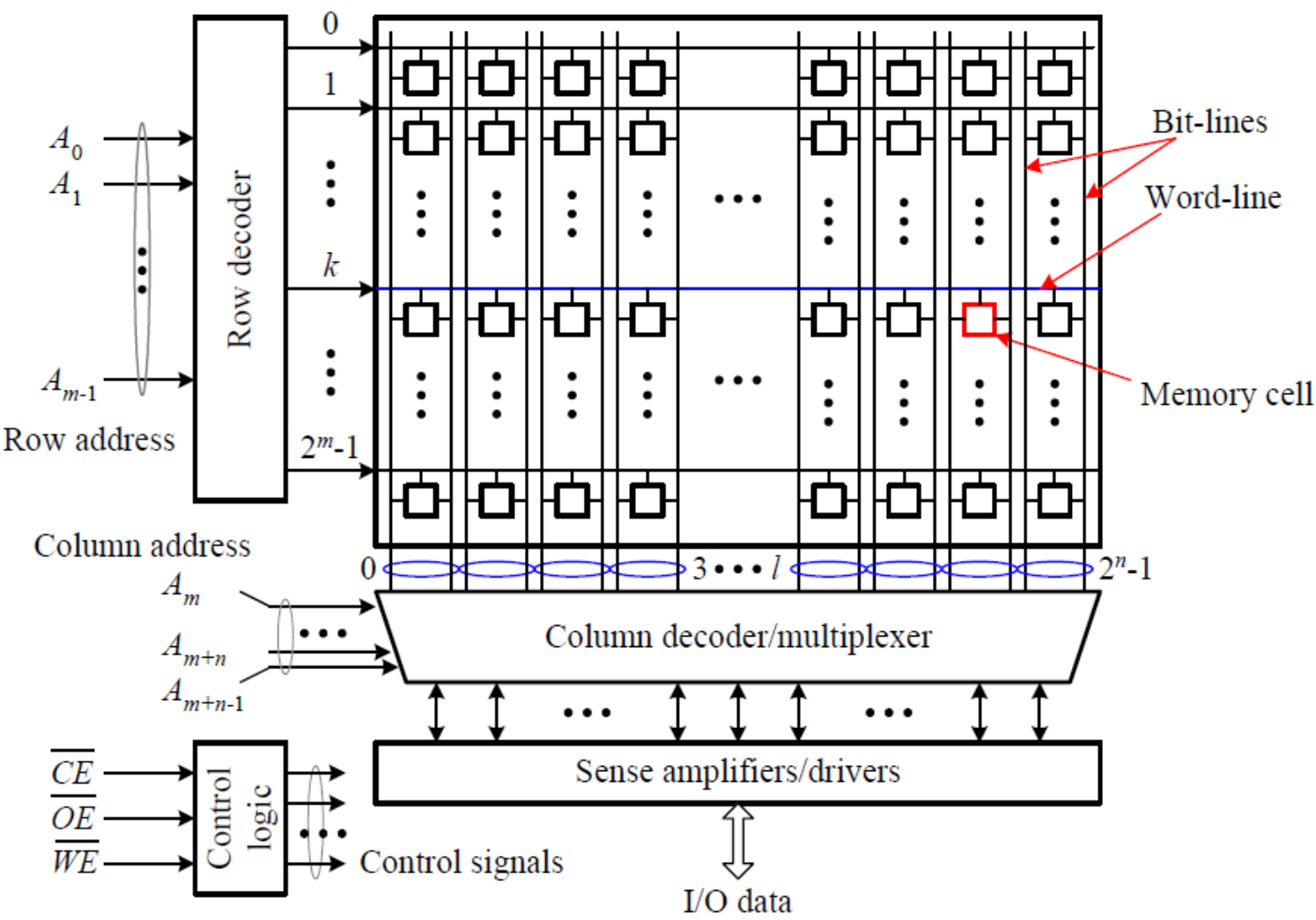

Typical Memory Architecture

- Storing in a memory matrix
 - A single element of a matrix stores one or more bit of information
 - We can activate a row by the **word line**, which is a part of the address generated by the row decoder.
 - The activated cells copy their content to the **bit line**
 - The other part of the address selects a single bit
- The sense amplifier is responsible for signal conditioning
 - It converts the low-level signal to a valid CMOS rail-to-rail signal
 - The transistors in the memory cells are very tiny (with the decrease of the cell size, the capacitance of the memory increases)
 - The input voltage on the sense amplifier is usually lower than 100mV, which has to be amplified

High capacity memory

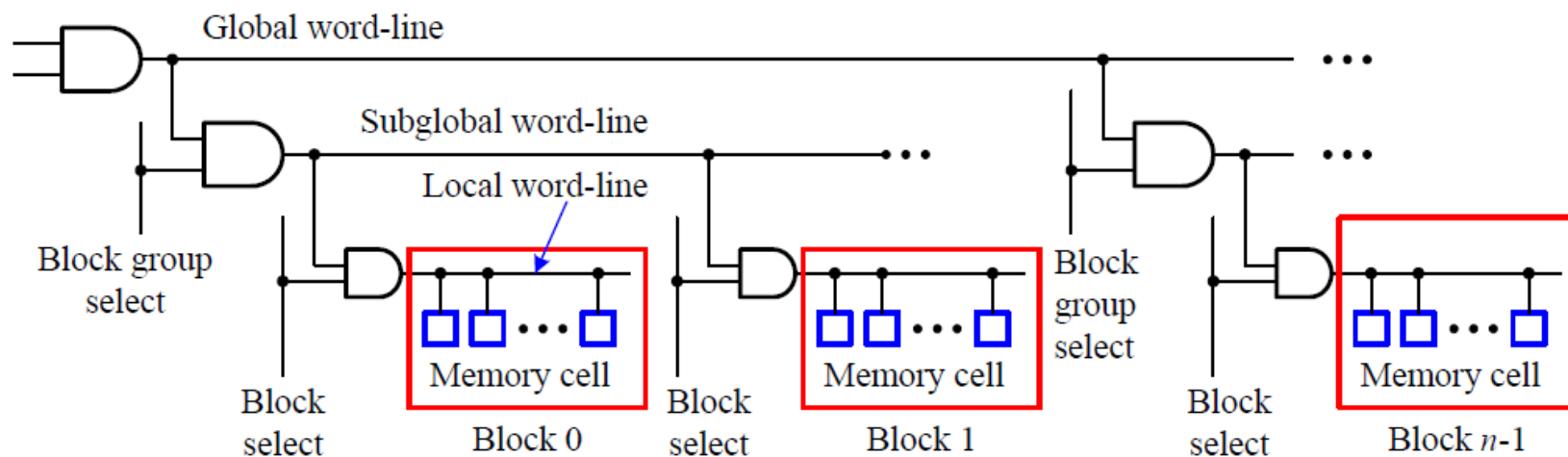

- If the number of rows is large, they are divided into partitions with hierarchical access
- The user can see **banks**




Budapest University of Technology and Economics
Department of Electron Devices

MOS transistor


in a detailed manner

Characteristics of MOS transistors

- In digital CMOS design a MOS transistor can be substituted with a 2-state switch
- Understanding the operation of memory cells requires greater understanding
- What we know so far?
 - The current flow between the drain and source can be controlled by the gate voltage
 - If the gate-source voltage is low, there is no current
 - If the gate-source voltage is higher than a certain value (V_T – threshold voltage) the transistor conducts current
 - This is enough knowledge for understanding the digital operation
 - Now we have to know what the relationship is between the gate-source voltage and drain-source voltage

 


MOS transistor

 

■ Important dimensions:

 - t_{ox} : oxide thickness (a few nm)
- L : length of the channel (14nm – a few μm)
- W : width of the channel (20nm – a few μm)



While $V_{GS} < V_T$, the transistor has very low current (subthreshold current, leakage current)

If $V_{GS} > V_T$, the current is proportional to $(V_{GS} - V_T)^2$

- $V_{GS} - V_T$ is usually denoted by V_{on}

The characteristic equation of MOS transistors

$$I_D = \frac{\epsilon_{ox} \mu_{eff}}{2t_{ox}} \frac{W}{L} (V_{GS} - V_T)^2 = \frac{\beta}{2} \frac{W}{L} (V_{GS} - V_T)^2$$

■ Where

- W is the width of the gate,
- L is the length of the gate,
- ϵ_{ox}/t_{ox} is the oxide capacitance per unit area,
- μ_{eff} is the mobility of the charge carriers in the channel,
- V_{GS} is the gate-source voltage,
- V_T is the threshold voltage of the device.

■ Designers can only alter the value of W and L

■ Wider transistors can conduct higher current

- They have lower (channel) resistance




Budapest University of Technology and Economics
Department of Electron Devices


Static RAM (SRAM)

Static RAM memory

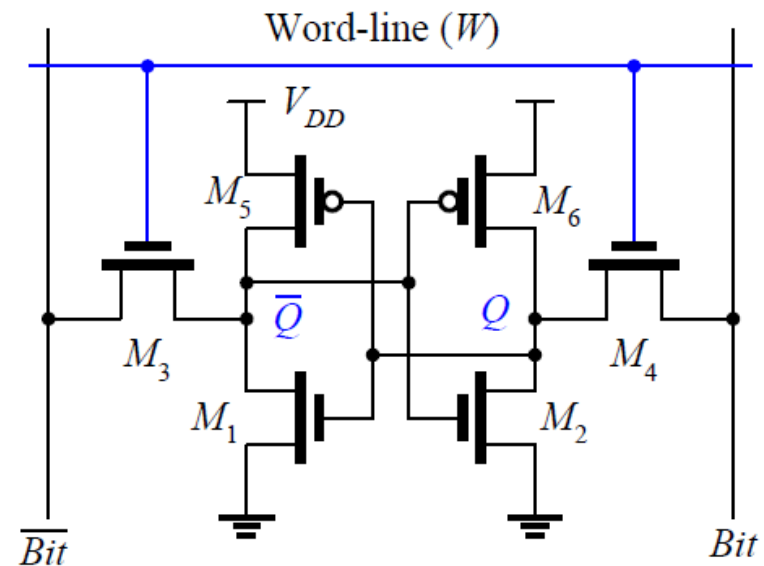
- It consists of 6 transistors
- It has two complementary bit lines
 - It is a differential logic element



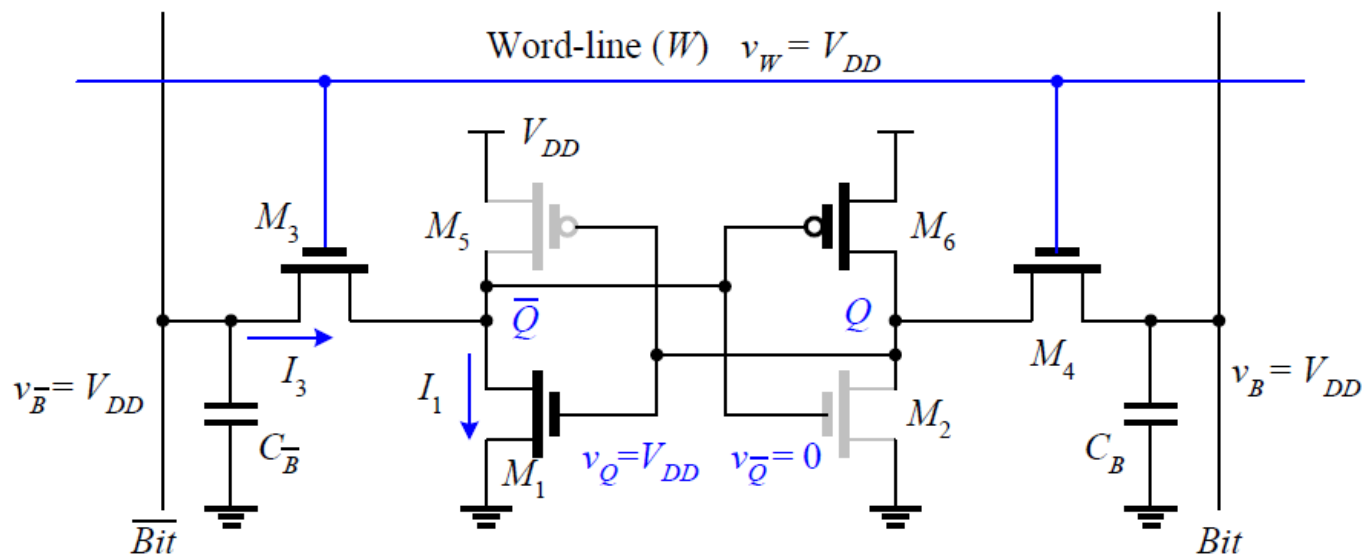
- Information is stored by two CMOS inverters in feedback.
- It is similar to SR latch, but the read/write is done through one transistor (not a complete (NAND) gate)
 - (In order to reduce the size of it)
- M_3 and M_4 transistors are called (access) transistors
- The operation of an SRAM cell seems simple (on the digital abstraction level), but it is more complicated



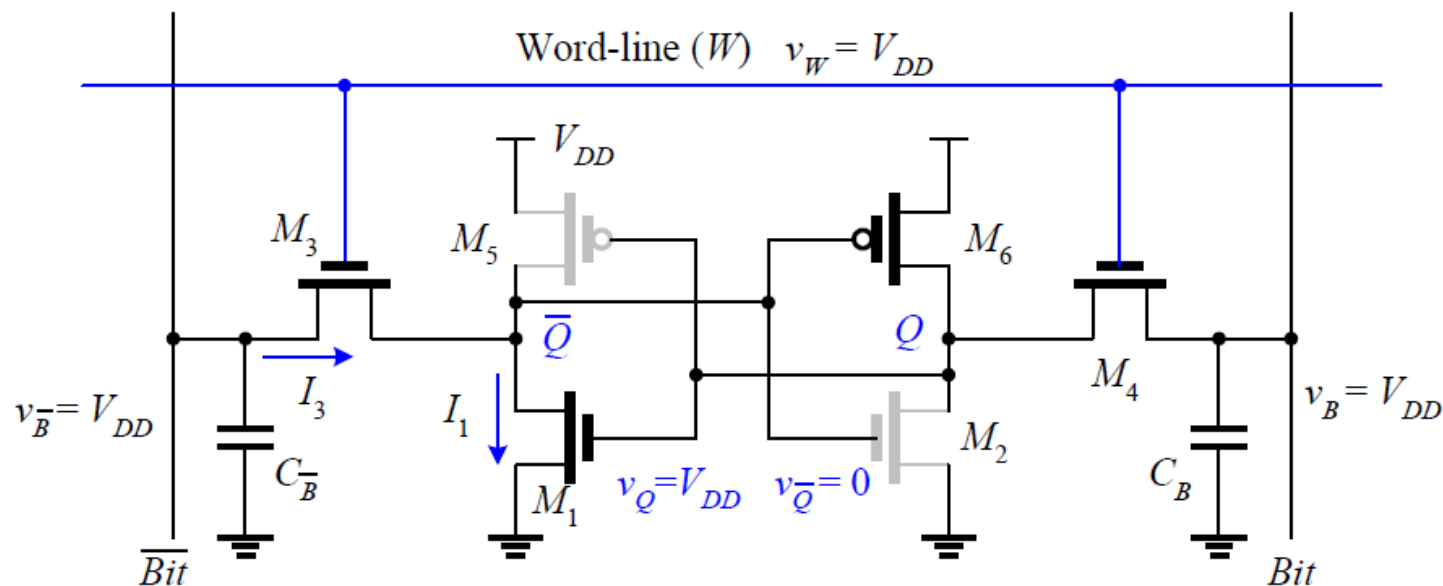- We assume that Q is logic 1
 - The bit-lines are precharged to the power supply voltage
- The transistor M_3 has a minimal channel width
- The NMOS transistors in the inverters have a two times wider channel width (they are “stronger”)
- At the beginning of the reading M_3 and M_1 conduct current, and the voltage level of \overline{Q} will increase




- $V_{\overline{Q}} = V_{DD} \frac{R_{M1}}{R_{M1} + R_{M3}} < V_{\text{COMP}} = \frac{V_{DD}}{2}$
- The change in voltage has to be lower than the threshold level of the gate, so that the content of the cell will remain unchanged
- The voltage level of the \overline{bit} line decreases to the half of the original value (around 100-200mV decreases is common) through the M_3 and M_1 transistors
- The sense amplifier can amplify it.

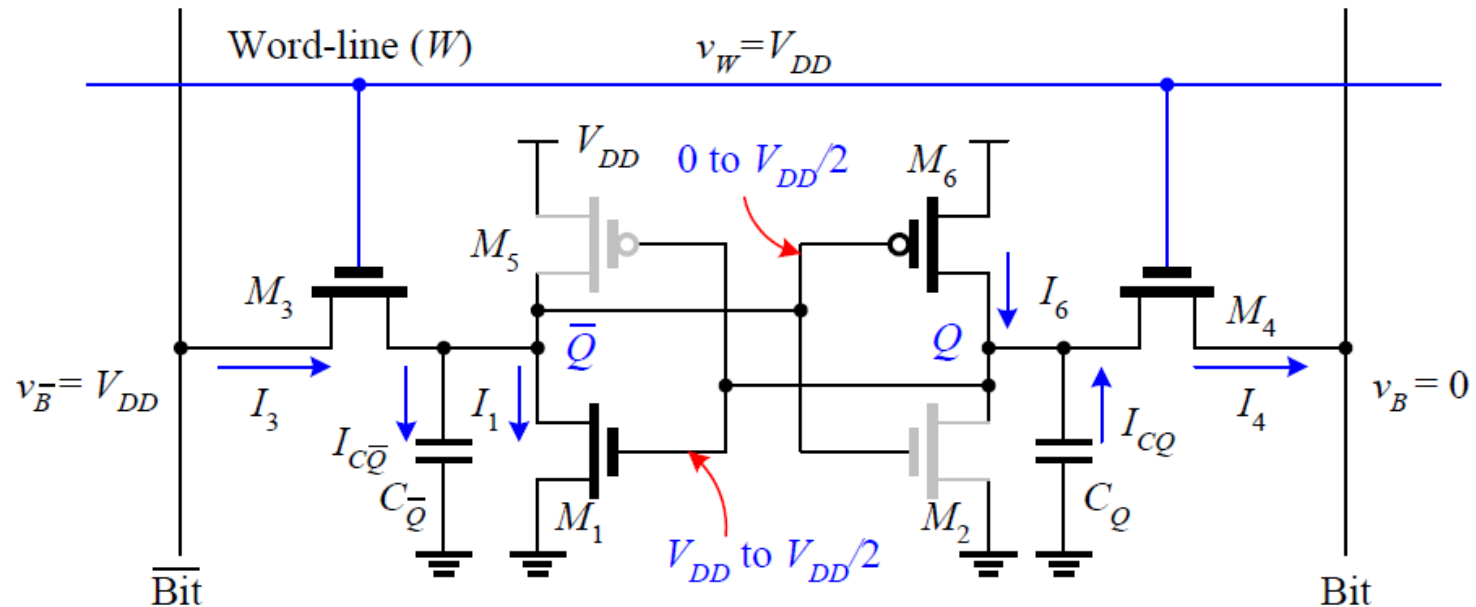


We assume the information in the memory cell is logic 1, and we have to write 0

 - The operation of the M_3 and M_1 transistors is similar to the reading case
- M_4 pulls the voltage level of Q below the threshold limit
- $V_Q = V_{DD} \frac{R_{M4}}{R_{M4} + R_{M6}} < V_{\text{COMP}} = \frac{V_{DD}}{2}$
- The current of M_1 decreases, M_5 conducts, and the flipflop flips



As we saw in the previous slide, a one bit-line is enough for reading

 - We can read from two cells using two bitlines
- In case of writing we need both bitlines
- Using “smart” timing we can read twice and write a bit in a cycle
- This is frequently used in CPU registers



- SRAM with dedicated read and write ports
 - It consists of 8 transistors




Budapest University of Technology and Economics
Department of Electron Devices

Dynamic RAM (DRAM)

Dynamic RAM cell

- The information is stored in the C_S capacitor, which is connected to the bitline by the M_1 transistor.
- C_S is typically 25-40fF (there are only ~100,000 electrons in the capacitor)
- The storage capacitors have a special 3D structure
 - Trench capacitance: a trench is etched in the Si. The walls are covered with oxide and filled with poli-Si.
 - Stack capacitance: several conducting layers are separated with thin oxide layers.

 


DRAM write and read

■ Writing to DRAM


- The word line is connected to VDD and the capacitor is charged to VDD or discharged to ground potential depending on the value of the bit-line

■ Reading from DRAM

 - The bit-line is precharged to half of the power supply voltage
- When the word line is activated, the capacitor is connected to the bit line
- After charge sharing, the voltage change of the bit-line is:
- $$\Delta V = \frac{C_S}{C_{BL} + C_S} V_{DD}/2$$
- The reading process is DESTRUCTIVE!




(a)

 


(b)

DRAM write and read

 - The voltage change is $\sim 20\text{-}50\text{mV}$
- The sensing amplifier has to determine the logic value of the cell from such a tiny change. This is a very difficult task
- The charge sharing discharges/charges the capacitor to a value from which the original logic value can no longer be determined so the cell has to be rewritten after each readout.




(a)

 


(b)

Refreshing DRAM

- The information stored in a cell fades over time due to the leakage current of the capacitor
- Thus the cells of a DRAM need to be refreshed periodically – typically every 2-4 ms.
- One line is refreshed at a time (it takes ca. 100-200 ns) (t_{RC})
 - **Burst refresh:** all the lines are refreshed in a run
 - **Distributed (hidden) refresh:** a counter stores the address of the most recently refreshed line and refreshing continues with the next line at every step.

 

Embedded DRAM

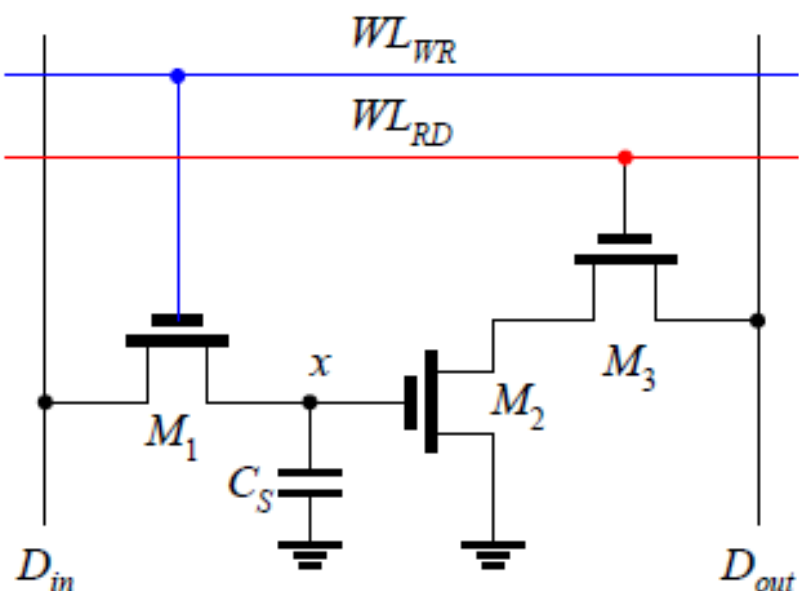- The single-transistor dynamic RAM requires special technology
 - In SoC devices only CMOS components are available
 - Instead of a storing capacitor we can use the parasitic capacitance of the M1 and M2 transistors
- 
- They are used in high capacitance cache memory circuits with hidden refresh
 - (smaller than SRAM)




Budapest University of Technology and Economics
Department of Electron Devices

CAM

Content Addressable Memory


Content Addressable Memory

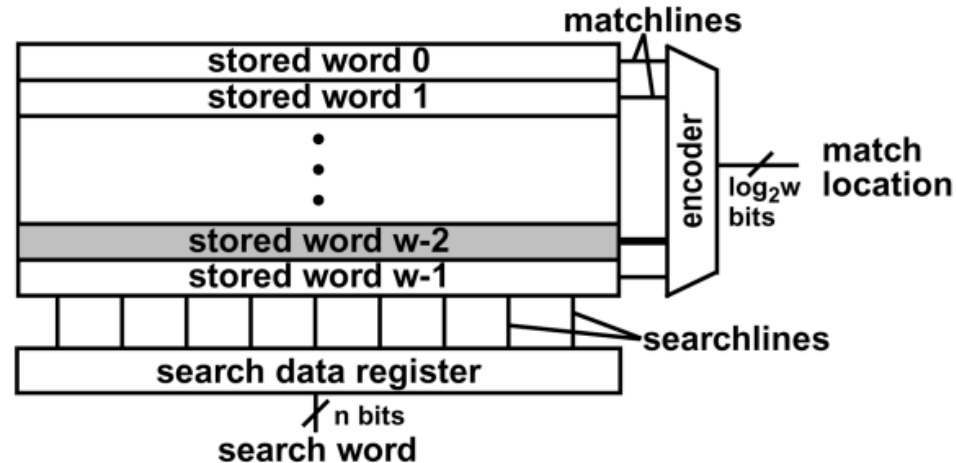

- It generates the address of the required information in a single clock cycle
 - It compares the content of the **search data register** to the parallel stored words
 - Only one will be activated from the matchlines, which gives the address back
- **The generated address corresponds to the content which is stored in the ordinary memory** (Hardware associative array)

CAM cell

 - A static RAM cell and 4 additional transistors
 - 4 transistors constitute the match circuitry
 - 10 transistors per cell
- If the input bit does not coincide with that stored in the SRAM, the match line is pulled down
 - “Miss-current” exists
- When a miss occurs, the CPU retrieves the data from the main memory



- Gábor TAKÁCS, takacs@eet.bme.hu



Budapest University of Technology and Economics
Department of Electron Devices



Newer memory technologies

Ferroelectric RAM (FRAM)
Magnetoresistive RAM (MRAM)



Ferroelectric RAM

■ Ferroelectric material

- The term is used in analogy to ferromagnetism
 - in which a material exhibits a permanent magnetic moment (so not an iron-based material)
- **Ferroelectricity** is a property of certain materials that have a spontaneous electric polarization
- It can be reversed by the application of an external electric field
 - lead zirconate titanate (PZT). ($\text{Pb}[\text{Zr}_x\text{Ti}_{1-x}]\text{O}_3$)
 - It has two stable states, because the oxygen atom can move to the center of the molecule
- The change in polarization causes charge movement (current)
- The idea was first published in 1952

  


FERAM single cell

 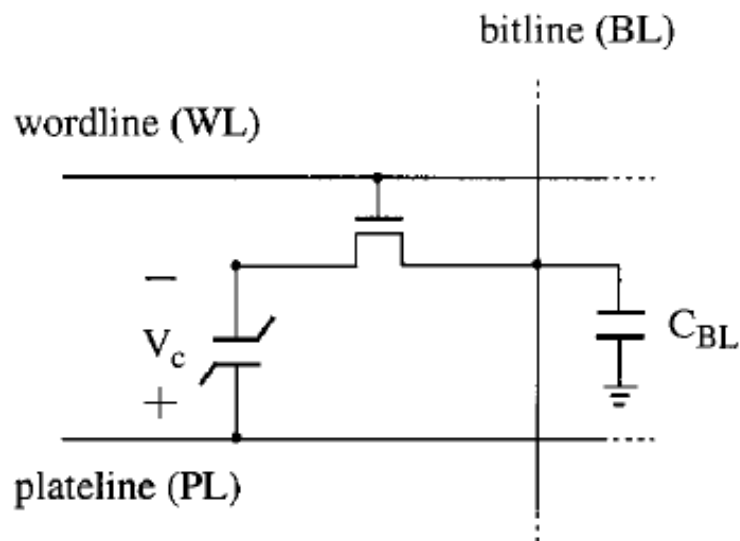


- It is similar to a DRAM cell, the storing dielectric material is the PTZ
- This is a capacitor with memory

FERAM reading

 

- The bitline has to be precharged
- We have to apply a pulse on the PL
- The voltage of the bitline changes (as in the case of DRAMs)
- The sense amplifier regenerates the signal
- The reading process is *destructive*


FERAM writing

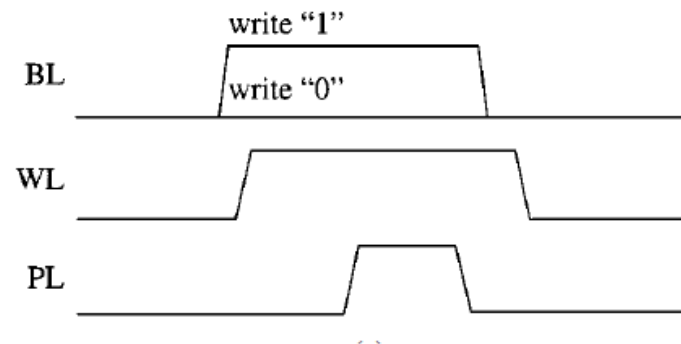


- Activate the word-line
- A pulse applied on PL writes the information of the BL into the cell

Magnetoresistive RAM

- Data in MRAM is stored by magnetic storage elements
- The elements are formed from two ferromagnetic plates
 - Each of which can hold a magnetization
 - They are separated by a thin insulating layer.
- One of the two plates is a permanent magnet set to a particular polarity
- The other plate's magnetization can be changed to match that of an external field
- The resistance of MRAM depends on the direction of the magnetization

 

MRAM single cell

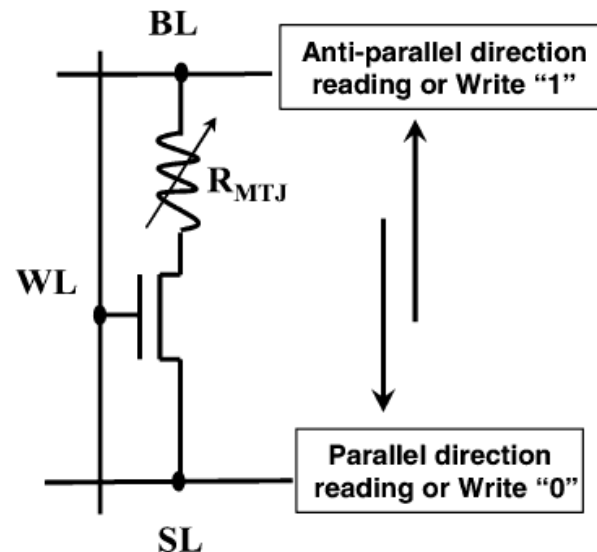

- Reading – measuring the current of the activated cell (non-destructive)
 - BL has low voltage, SL is connected to ground
- Writing – High voltage applied between the bitline and the wordline
 - The value of the stored bit depends on the direction of the applied voltage
 - $BL=0V$, $SL=VDD$ or $BL=VDD$, $SL=0V$

Attribute	FRAM	MRAM
Technology	1 transistor – 1 ferroelectric capacitor (1T – 1FRC)	1 transistor – 1 magnetic tunnel junction (1T – MTJ)
Read	Destructive	Non-destructive
Read Cycle Time	90ns	35ns
Read Access Time	60ns	35 ns
Write Cycle Time	90ns	35ns
Write (CE)	60ns	35ns
Fatigue	Known wear-out mechanisms 10^{14} Read / Write	No wear-out. Infinite Read / Write
Imprint	Increases with temperature and decreasing operating voltage	No Imprint
High Temperature Data Retention	Degrades above 85°C	20 years at 125°C (continuous)
Manufacturing	Complex – O ₂ ambient >650°C process, H ₂ sensitivity.	Standard BEOL CMOS processing
Scalability	Need 3D structures at 65nm. Imprint becomes more of an issue.	Fully Scalable

- Imprint is the preferential polarization state from previous writes to that state
- Fatigue is the increase of minimum writing voltage due to loss of polarization after extensive cycling.



Budapest University of Technology and Economics
Department of Electron Devices


RAM memory chips - Examples

Based on google search result.

IDT 7006S/L – Dual-port static RAM

- Two ports, 16k x 8 bit SRAM
 - Left and right ports, fully symmetrical
 - Allows simultaneous reads of the same memory location
- On-chip arbitration
- HW semaphore signaling
 - Concurrent accesses of different ports handled by the hardware
- Fully asynchronous operation

Waveform of Read Cycles⁽⁵⁾

 


2739 drw 07

Micron - MT46V64M8

- 512MBit, 64M x 8bit.
 - Power supply: 2.5V
 - DDR 400 – Internal, pipelined double-data-rate
 - 4 banks
 - Programmable burst lengths: 2, 4 or 8
 - Auto refresh: 64ms (8192 clock cycles)
 - CL (CAS / READ latency) – 2, 2.5, 3
 - Row address: A0-A12 (8k), Column address: A0- A9, A11 (2k)
 - Bank address: BA0, BA1
- It is very complicated to use


DDR SDRAM example - Reading

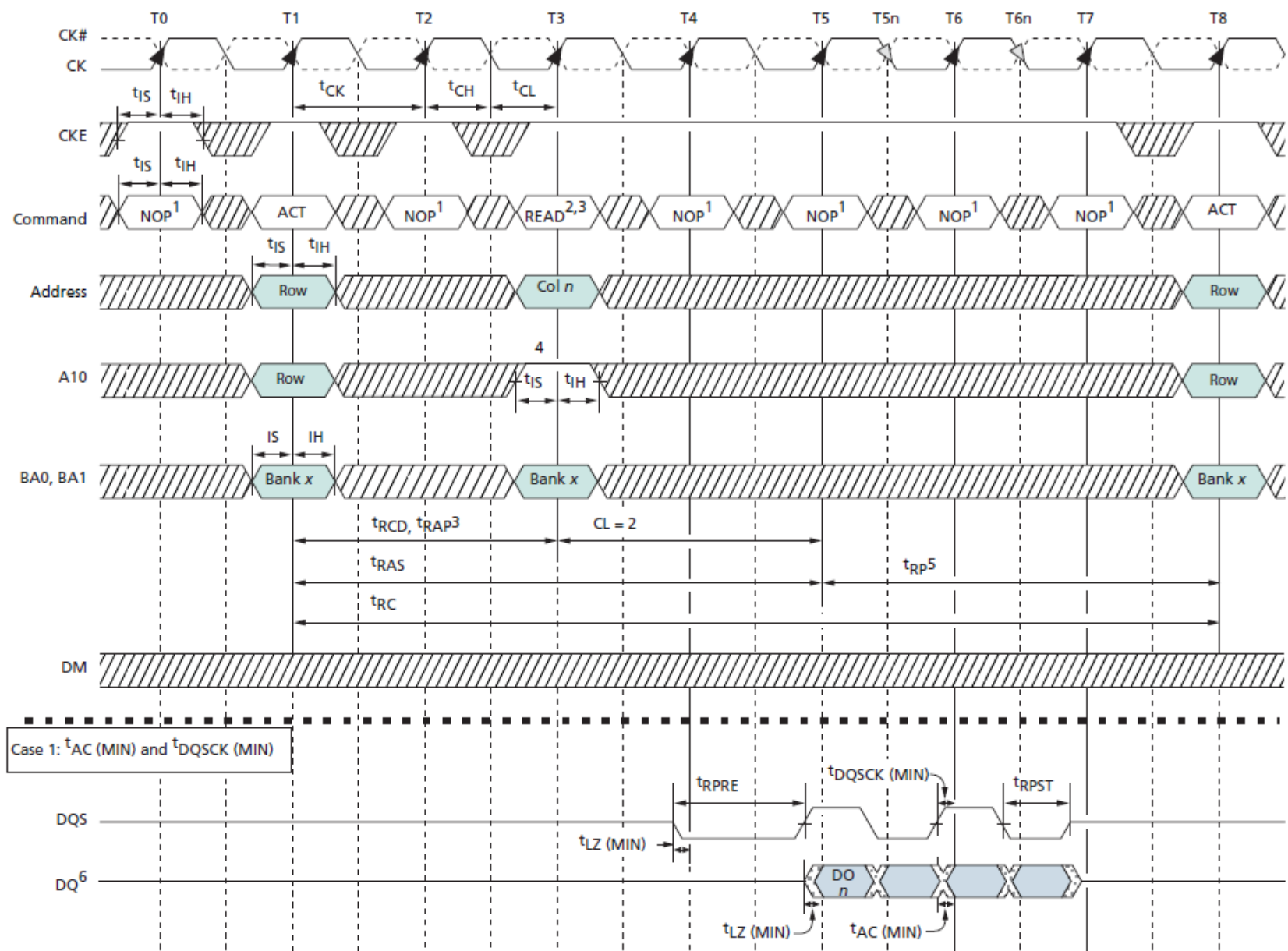


LAPIS Semi, **MR45V032A**

- 32k(4,096-Word 8-Bit) FeRAM (Ferroelectric Random Access Memory) SPI
- 4k× 8bit
- Power supply: 2.7-3.6V, (3.3V typical)
- Operating frequency: 15MHz
- Data retention: 10 years
- Read/write tolerance: 10^{12} cycles/bit
- Communication:
 - SPI (Serial Peripheral Interface)

8-pin plastic SOP

 

FERAM

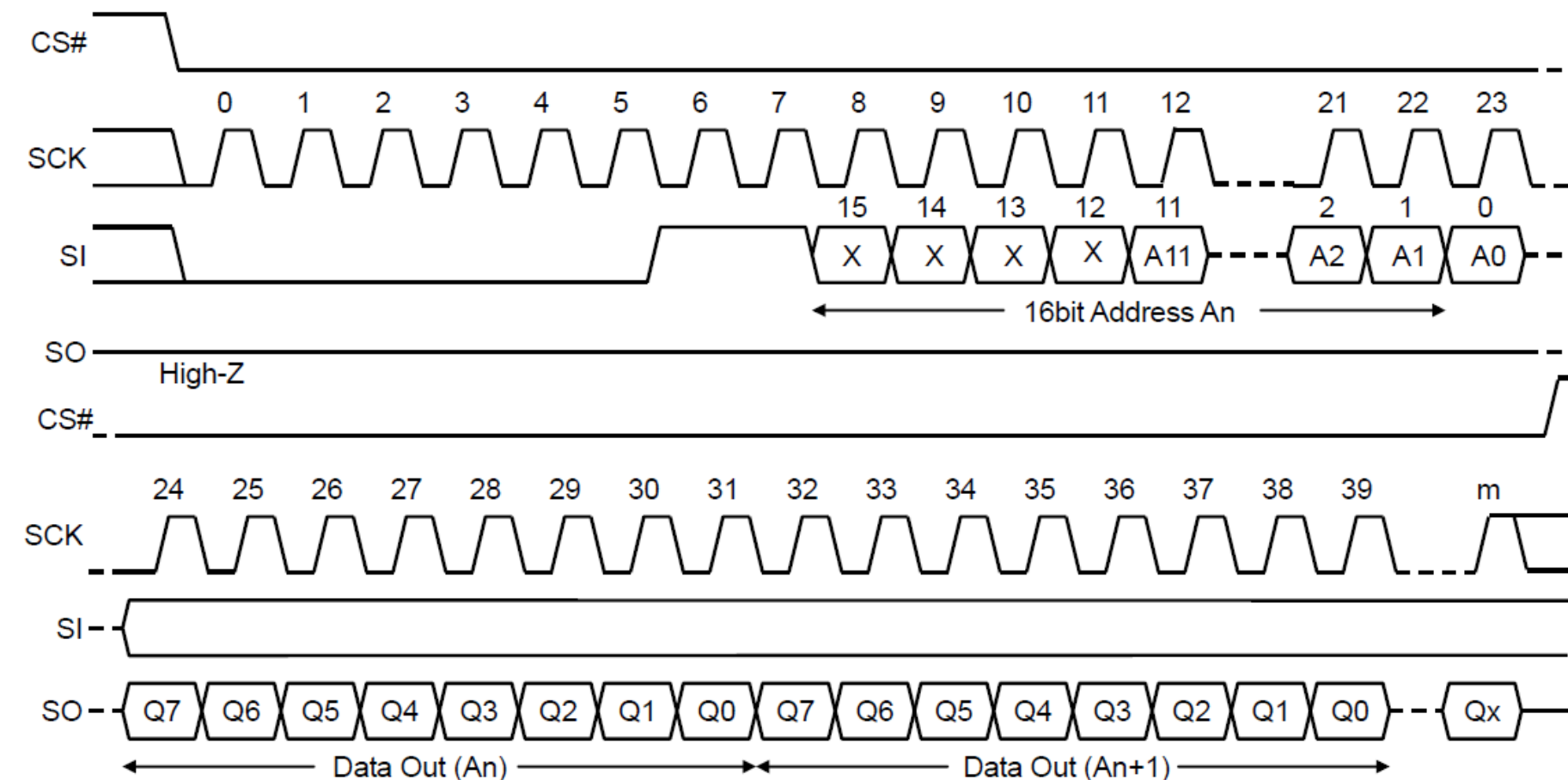

0x03 represents the READ command, and it is followed by the 16-bit starting address