

# Technology of IT Devices

## Lecture 3

- Circuits of Boolean algebra
- Basic properties of digital logic

# Circuits of Boolean algebra

## ■ Boolean algebra

- Boolean algebra is the branch of algebra in which the values of the variables are the truth values true and false, usually denoted 1 and 0 respectively.


- Set of values  $x \in \{0,1\}$
- Basic operations  $\neg \wedge \vee$  (NOT (negation), AND (conjunction), OR (disjunction))

## ■ Physical quantities are assigned to the elements of the set of values, usually the voltage level.

- (It can be current or voltage difference – in high speed logic circuits)
- Generally,  $V_H$  is assigned to logical 1, and  $V_L$  is assigned to logical 0
- Mostly  $V_H$  is equal to the positive supply voltage, and  $V_L$  is the ground
- The voltage difference between  $V_H - V_L$  is the so-called **swing**
- The difference between the positive power supply (VDD) and the ground (0V) is called **RAIL**
  - (The positive power supply and the ground have the widest wires in a circuit, and they seem like a rail - hence the name)

 
## Transfer characteristic

- The relationship between the input and output of an electronic system, especially as depicted graphically
- The transfer characteristic of an inverter is shown on the right
- The output is the negated value of the input.  $V_L = f(V_H)$  and  $V_H = f(V_L)$
- The proximity of the supply voltage (VCC) is logic 1 or HIGH,
- and the proximity of the ground potential is logic 0 or LOW.
- The switching threshold,  $V_M$ , is defined as the point where  $V_{in} = V_{out}$ .



 
# Noise immunity

- The same logic level is assigned to a wide range of input voltage.
  - When the noise level is lower than the limit it cannot appear on the output (the circuit can **reject** it)
- The characteristic has 3 regions
  - the extremes are flat, so the changes of input voltage cause only small changes on the output.
    - safe logic-level tolerances can be defined
  - In the central region the characteristic is steep.
    - (The amplification is high, so  $A = \frac{dV_{OUT}}{dV_{IN}}$  high)
    - small changes of input voltage cause high changes on the output


 
# Signal regeneration



- During digital signal processing, digital signals regenerate



- In the figure above the transfer function of  $f(V)$  and its inverse function  $f_{inv}(V)$  can be seen
- The digital circuit converts the „weak”  $V_0$  signal to  $V_1$ ,  $V_2$ ,  $V_3$  voltages
  
## Example: signal regeneration (circuit simulation)

- This is just a textbook example, the situation is even better in the real world!
  - A weak signal (lower than the nominal value by 1.5V) is applied on the input of the first inverter, and a  $1V_{pp}$  noise signal is superimposed
  - On the output of the first inverter the voltage is lower than the nominal value by 0.5V, and the noise level is reduced by the factor of  $\sim 3$ .
  - The output of the second inverter is almost perfect.
  - The level and the shape of the signal is completely regenerated



## Example for signal levels

### ■ Fairchild, 74HC00

DC Electrical Characteristics (Note 4)								
Symbol	Parameter	Conditions	V <sub>CC</sub>	T <sub>A</sub> = 25°C		T <sub>A</sub> = −40 to 85°C	T <sub>A</sub> = −55 to 125°C	Units
				Typ	Guaranteed Limits			
V <sub>IH</sub>	Minimum HIGH Level Input Voltage		2.0V		1.5	1.5	1.5	V
			4.5V		3.15	3.15	3.15	V
			6.0V		4.2	4.2	4.2	V
V <sub>IL</sub>	Maximum LOW Level Input Voltage		2.0V		0.5	0.5	0.5	V
			4.5V		1.35	1.35	1.35	V
			6.0V		1.8	1.8	1.8	V
V <sub>OH</sub>	Minimum HIGH Level Output Voltage	V <sub>IN</sub> = V <sub>IH</sub> or V <sub>IL</sub>  I <sub>OUT</sub>   ≤ 20 μA	2.0V	2.0	1.9	1.9	1.9	V
			4.5V	4.5	4.4	4.4	4.4	V
			6.0V	6.0	5.9	5.9	5.9	V
		V <sub>IN</sub> = V <sub>IH</sub> or V <sub>IL</sub>  I <sub>OUT</sub>   ≤ 4.0 mA  I <sub>OUT</sub>   ≤ 5.2 mA	4.5V	4.2	3.98	3.84	3.7	V
			6.0V	5.7	5.48	5.34	5.2	V
V <sub>OL</sub>	Maximum LOW Level Output Voltage	V <sub>IN</sub> = V <sub>IH</sub>  I <sub>OUT</sub>   ≤ 20 μA	2.0V	0	0.1	0.1	0.1	V
			4.5V	0	0.1	0.1	0.1	V
			6.0V	0	0.1	0.1	0.1	V
		V <sub>IN</sub> = V <sub>IH</sub>  I <sub>OUT</sub>   ≤ 4.0 mA  I <sub>OUT</sub>   ≤ 5.2 mA	4.5V	0.2	0.26	0.33	0.4	V
			6.0V	0.2	0.26	0.33	0.4	V
I <sub>IN</sub>	Maximum Input Current	V <sub>IN</sub> = V <sub>CC</sub> or GND	6.0V		±0.1	±1.0	±1.0	μA
I <sub>CC</sub>	Maximum Quiescent Supply Current	V <sub>IN</sub> = V <sub>CC</sub> or GND I <sub>OUT</sub> = 0 μA	6.0V		2.0	20	40	μA


# Robustness

- Digital logic circuits are **ROBUST**
- Within given limits, they are not sensitive to
  - Changes in the power supply
  - Changes in the ambient temperature
  - Mismatches of component parameters
  - etc.



 
## Fan-out

- Fan-out is a term that defines the maximum number ( $N$ ) of digital inputs that the output of a single logic gate (of the same type) can feed.
- Eg. FO4 – 4 logic gates can be connected to the output


 
# Propagation delay

- When an input signal of a logic gate is changed, there is a propagation delay before the output of the logic gate changes.
  - This is due to capacitive loading at the output.
  - The propagation delay ( $t_p$ ) is measured between the 50% transition points of the input and output signals.
  - Rise time ( $t_r$ ) and fall time ( $t_f$ ) are measured between the 10% and 90% transition points




## Propagation delay

- The length of the positive and negative edge can be different.
  - $t_{pHL}$  – delay of high to low transition
  - $t_{pLH}$  – delay of low to high transition
- The delay is the average value of these two values
  - $t_{pd} = \frac{t_{pLH} + t_{pHL}}{2}$
- The **critical path** is defined as the path between an input and an output with the maximum delay.
- The critical path determines the speed of the whole digital circuit
 
## Ring oscillator

- Ring oscillator: an odd number (N) of inverters connected in series with the output connected to the input.
- The figure below depicts a practically used version.
  - The first inverter is replaced by a NAND gate.
  - If EN input is high, the NAND gate acts like an inverter
  - This circuit has no stable states, it oscillates
  - The frequency of the oscillation is a function of the propagation delay:  $T = 2Nt_{pd}$ 
    - The pair delay can be measured with a ring oscillator



# Power and energy

- Power = It is the amount of energy consumed per unit time.
  - SI unit: Watt (J/s)
  - Two important parameters
    - Average power:  $P_{av} = \frac{V_{DD}}{T} \int_0^T I(t) dt$
    - Peak power:  $P_{peak} = V_{DD} I_{peak} = V_{DD} \max(I(t))$
    - where  $V_{DD}$  is the supply voltage of the gate,  $I$  is the current
- The power consumption can be divided into two parts
  - Static consumption – It is always present
  - Dynamic consumption – at every switching event. It depends on the frequency and the switching probability.
- Energy
  - $E = \int P(t) dt$
  - SI unit: Joule (kWh)

## Power–delay product (PDP)

- The power–delay product is correlated with the energy efficiency of a logic gate or logic family
  - In current technologies capacitive dissipation is by far dominant
- The power-delay-product (PDP) is a measure of energy and is defined by the product of the average power ( $P_{ave}$ ) and the gate delay  $t_p$ 
  - PDP is  $C_L V_{DD}^2 f_{max} t_p$  which is equivalent to  $C_L V_{DD}^2 / 2$ .
  - This expresses the average energy consumed per switching event.
  - This is a metric for digital designs

## Example

- Lets assume that we have a microprocessor, where the dominant factor is the dynamic power consumption. Lets decrease the frequency by the factor of 2. Can we extend the battery lifetime in this way?
- Solution:
  - The power at the half frequency is:  $P' = \frac{P}{2}$
  - The runtime of the same program is double:  $\Delta t' = 2\Delta t$
  - Energy consumption:  $E' = P'\Delta t' = 0.5P \cdot 2\Delta t = E$
  - So the energy consumption is the same, but we have to wait twice as much time for the result

# CMOS circuits


## ■ Complementary MOS

- The words "complementary" refer to the fact that the typical design style with CMOS uses complementary pairs of p-type and n-type MOS transistors for logic functions.
- **rail-to-rail levels**: the logic levels are exactly equal to the supply levels
  - $V_H = V_{DD}$ ,  $V_L = 0V$
- Static (steady-state) current consumption is very low (almost zero).
- Propagation delay of positive and negative edges are equal
- Very low sensitivity to supply voltage ripple.
- Area occupied by the logic gates is much smaller than other types
  - We can integrate more components on a unit surface





 
# nMOS and pMOS transistors as switches

- nMOS
  - In case of logical 0: open switch (does not conduct current)
  - In case of logical 1: closed switch (conducts current)
- pMOS
  - logical 0: conducts current,
  - logical 1: does not conduct current
- The symbol of pMOS transistor has a circle at the gate terminal



   
# Schematic of CMOS inverter

- CMOS inverter: an n-MOS and a p-MOS
  - At any time only one of them is open



 
# Transfer characteristic curve of the inverter

- The nMOS transistor conducts current when the input voltage is higher than the threshold voltage.
- The pMOS conducts current when the input voltage is lower than  $V_{DD} - V_T$
- There is a region (in case of high supply voltage) where both transistors conduct current,  $V_T \leq V_{IN} \leq V_{DD} - V_T$




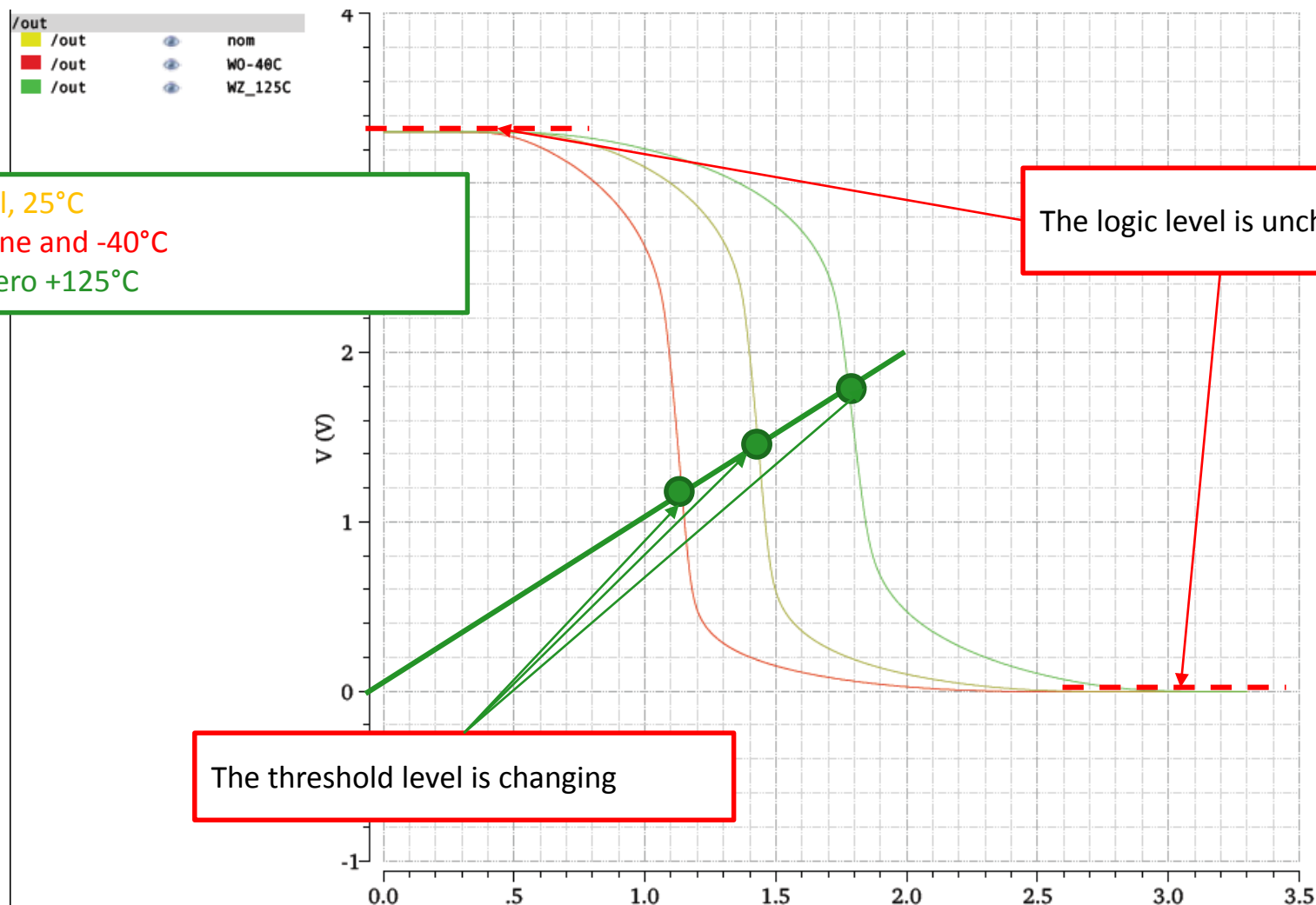
# Simulated transfer characteristic of CMOS inverter


  
## Load of CMOS inverter (gate)

- The load is capacitive
  - Transistors have internal parasitic capacitances (intrinsic capacitances)
  - Capacitances of interconnect wires – This is dominant in a modern technology





## Propagation delay

- The propagation delay is determined by the charge and discharge of the (parasitic) capacitances
- The higher the capacitances, the higher the delay
- It the power supply voltage is higher, the delay is lower (due to the higher charging and discharging).
  - (To be more precise:  $Q = CV_{DD}$ , but  $I \sim V_{DD}^2$ )
  - How does the overvolting help us to overclock?
    - To improve a computer performance we can increase the clock frequency
    - It is necessary to increase the core voltage as well to maintain the signal levels
  
# Power

- Static power consumption.
  - It is important in modern circuits
    - Sub-threshold currents,
    - Leakage currents of the pn-junctions,
    - Tunnel current through the gates
- Dynamic consumption – at every switching event:
  - The current that flows during transitions
  - It is proportional to the clock frequency and the activity of the circuit.



## Dynamic current consumption

- The dynamic current consumption is the sum of two factors:
  - Transition current: both transistors are open during the transition between logic states
  - Charge pumping: during a positive edge the load capacitance is charged to logic 1 by the pMOS, during a negative edge the load capacitor is discharged through the nMOS.
- The dominant factor is the charge pumping.



# Charge pumping

- The output capacitance is loading:

- The stored energy in the capacitor:


$$E_C = \frac{1}{2} C_L V_{DD}^2$$

- The energy needed from the power supply:

$$E = \int_0^{\infty} I(t) V_{DD} dt = \int_0^{\infty} C \frac{dV}{dt} V_{DD} dt = C V_{DD} \int_0^{V_{DD}} dV = C V_{DD}^2$$

Half of the energy is stored in the capacitor, the other half is lost (dissipated by the pMOS transistor).

 - During the discharge event the charge is removed by the nMOS transistor (no energy is needed from the power supply).



## Charge pumping

- During transitions charge is pumped into and out of the load capacitor, i.e. charge is pumped from the supply to the ground
- If the circuit switches at frequency ( $f_{sw}$ ) per unit time ( $T$ ), the number of switch transitions is

$$T f_{sw}$$

- The required power:

$$P = \frac{E}{T} = f C V_{DD}^2$$

The power consumption of a CMOS digital circuit is proportional to  $f$  and  $V_{DD}^2$

$$P \sim f V_{DD}^2$$

## Dynamic Voltage Frequency Scaling

- The frequency of a microprocessor can be automatically adjusted "on the fly" by the OS.
  - Higher clock frequency requires higher core voltage
  - At lower frequencies less voltage is enough
  - The power consumption is a square function of voltage
- Calculate the power ratio of the P0 (1.6GHz@1.484V) and the P5 (600MHz@0.956V) states of a Pentium M processor

$$\frac{P_0}{P_5} = \frac{1.6}{0.6} \left( \frac{1.484}{0.956} \right)^2 = 6.4$$

- According to the Intel datasheet, the ratio is 4.2. The difference is due to other power consumption factors